TABLE OF CONTENTS

UNIT: I ELECTROSTATICS & D.C CIRCUITS

1.0	Electrostatics	1
1.1	Electrostatic force	1
1.2	Electric field	1
1.2.1	Electric Field Line	2
1.2.2	Properties of Electric field lines	2
1.3	Electric Flux	3
1.4	Electric flux density	3
1.5	Electric field intensity	3
1.6	Electric Potential	3
1.7	Permittivity of Free Space(ε_o)	4
1.7.1	Absolute permittivity:(ε)	4
1.7.2	Relative permittivity :(ε_r)	4
1.8	Capacitor	4
1.8.1	Basic Construction	5
1.8.2	Working of Capacitor	5
1.9	Coulomb's law of electrostatics	6
1.10	Capacitance	7
1.11	Relationship between the voltage, capacitance and charge	7
1.12	Capacitors connected in series	7
1.13	Capacitors connected in parallel	8
1.14	Energy stored in a capacitor	9

1.15 Introduction 15
1.16 Electrical Circuit 16
1.16.1 Conductors 16
1.16.2 Insulators 16
1.16.3 Semiconductors 17
1.16.4 Superconductors 17
1.16.5 Newton 17
1.16.6 Joule 17
1.17 Electricity 17
1.18 Electrical Charge 17
1.18.1 Coulomb 18
1.19 Current 18
1.19.1 Ampere 18
1.20 Electro Motive Force(E.M.F) 19
1.21 Potential Difference (p.d) 20
1.21.1 Difference between E.M.F and Potential difference (p.d) 20
1.22 Electrical power 20
1.23 Energy 21
1.24 Electrical Circuit Elements 21
1.24.1 Classifications of Electrical Circuit Elements 21
1.24.2 Passive Elements 21
1.24.3 Active Elements 21
1.25 Resistance 22

3.20.1 Phase lag 179
3.20.2 Phase lead 180
3.20.3 Phasor diagram 180
3.20.4 Reference Phasor 181
3.20.5 Angular velocity 181
3.21 Impedance(Z) 181
3.22 Inductive Reactance(XL) 181
3.23 Capacitive Reactance(XC) 182
3.24 Admittance(Y) 182
3.25 Conductance(G) 182
3.26 Susceptance (B) 182
3.27 Power(P) 183
3.27.1 Real power(P) 183
3.27.2 Reactive Power(Q) 183
3.27.3 Apparent Power(S) 183
3.28 Power Factor (cos) 183
3.29 Voltage and Current Relationship in Pure Resistance 184
3.30 Voltage and Current Relationship in Pure Inductance 185
3.31 Voltage and current relationship in capacitance 188
3.32 Series r_l circuits 190
3.33 Series r_c circuits 193
3.34 Series r_{lc} circuit 196
3.35 Power triangle 199

3.35.1 Active Power 199

3.35.2 Reactive Power 199

3.35.3 Apparent Power 200

3.35.4 Power Factor 200

UNIT : IV RESONANT CIRCUITS

4.0 Introduction 248

4.1 Resonance 248

4.2 R.L.C Series Resonance Circuit 249

4.3 Resonance frequency 249

4.4 Effect of varying frequency on Inductive reactance (XL) 250

4.5 Effect of varying frequency on capacitance reactance (XL) 251

4.6 Effect of varying frequency on Capacitive reactance (X_C) 251

4.7 Characteristics of series resonance 252

4.8 Q-factor(or) Quality factor 253

4.8.1 Importance of Q-Factor 254

4.8.2 Q-Factor and Resonance curve 254

4.9 Bandwidth (BW) 255

4.9.1 Derive Q factor from Band width and Resonant frequency 255

4.10 Selectivity 256

4.10.1 Importance of Selectivity 256

4.11 Accept or Circuit 256

4.12 Properties of Series Resonance 256

4.13 Parallel resonance 266

4.13.1 Vector diagram 267

4.14 Q-factor

4.15 Condition for Parallel Resonance

4.16 Resonance Frequency

4.17 Impedance at Resonance

4.18 Graphical Representation

4.18.1 Characteristics of Parallel Resonance

4.19 Reject or circuit

4.20 Properties of parallel resonance

4.21 Comparison of Series and Parallel Resonant circuit

4.22 Application of Resonance

UNIT:V THREE PHASECIRCUITS

5.1 Three Phase Systems 282

5.1.1 Expressions for Voltage and Current in a three phase system 283

5.1.1 Expressions for Voltage and Current in a three phase system 283

5.2 Necessity of Three Phase system 283

5.2.1 Advantages of three phase system 284

5.3 Terms and Definition 285

5.3.1 Phasor Representation 285

5.3.2 Phase sequence 285

5.3.3 Negative sequence 286

5.3.4 Phase voltage 286

5.3.5 Line voltage 286

5.3.6 Phase current 287

5.3.7 Line current 287

5.4	Concept of balanced and unbalanced load	287
5.4.1	Balanced load	287
5.42	Unbalanced load	287
5.5	Methods of three phase connection	287
5.5.1	Star or Why Y connection	288
5.5.2	Delta Δ connection	288
5.6	Relationship between line current and phase current, line Voltage and phase voltage in a star connected system.	289
5.7	Relationship between line current and phase current, line voltage and phase voltage in a delta connected system.	291
5.71	Advantages of star connection	293
5.72	Advantages of delta connection	294
5.8	Floating neutral point	294
5.8.1	Power Measurement by single wattmeter method	294
5.9	Power Measurement by two wattmeter method	295
5.10	Effects of Load P.F on Wattmeter Readings	297
5.11	3 Phase, 4 wire star connected system	297